

University Of Texas At Austin

Schematic Name: Lab 7: Soundtrack Device


Author(s): Kevin Yee and Stefan Bordovsky

Date: 3/19/2017

Semester: Spring 2017





<http://users.ece.utexas.edu/~valvano/HowToDesignEnclosureMakerspace.htm>
This PCB will go into a Lab9Box, WoodBox and WoodBox2

ps t 3 V

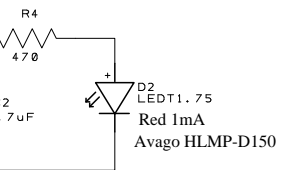

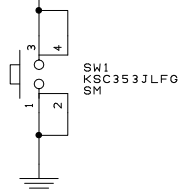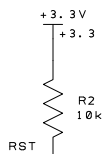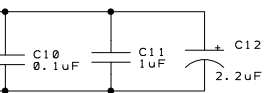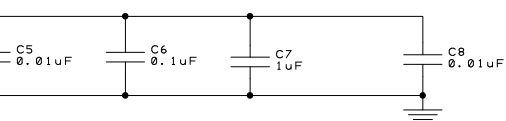
7-3.3 if 100<I<500mA

4C123 LaunchPad
M4C123 Connected LaunchPad)
bugger



2-ND
(e)

MHZ-B2-T

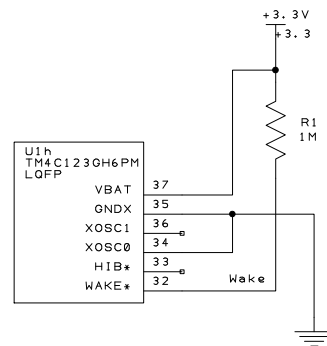

University Of Texas At Austin

Schematic Name: Lab 7: Power Clock JTAG

Name(s): Kevin Yee and Stefan Bordovsky

Date: 3/19/2017

Semester: Spring 2017